

HOME WORK 02

TASK : Smart Gate System

You are the **Electronic Engineer** in the **SUN Construction PVT LTD** and you were assigned to design an **Auto Gate System** for a Car Park. The gate must open when a car is **15 cm** away from the gate, and when the gate opens the system must light the **Blue Bulb**, otherwise the **Red Bulb**. Use the **Arduino Development Board** for design of this system.

Assignment Questions

01. What are the sensor components you need to implement this system?
02. Draw the wiring diagram.
03. Create the circuit and simulate in TinkerCad and send me through WhatsApp.

Good Luck !
